

# Meow Repellent

## Parts




1. Main board
2. Ultrasonic Sensor
3. Display
4. Nozzle
5. Pump
6. Water bottle




## Connections:

### Ultrasonic Sensor to Mainboard

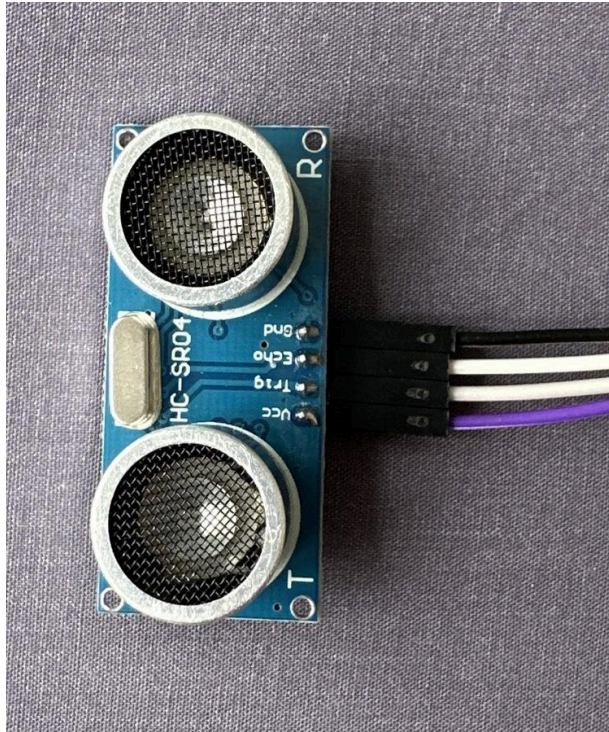


Ultrasonic Sensor

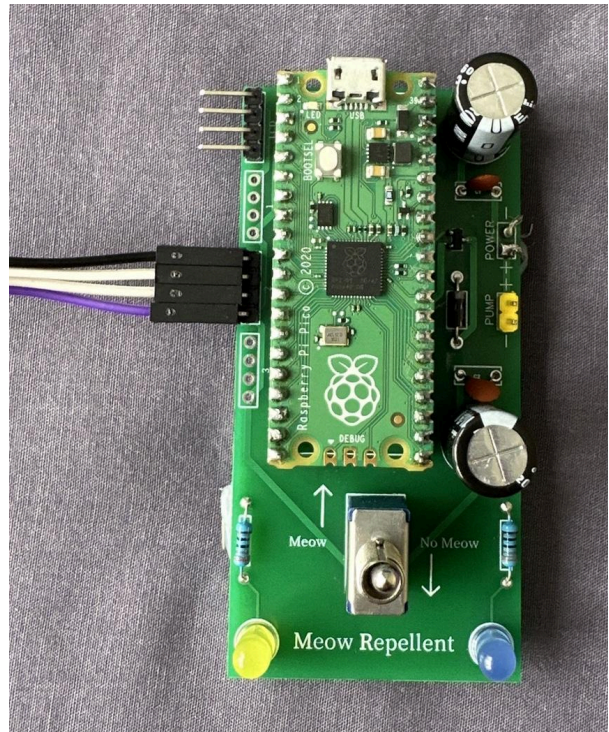


Mainboard

### Display to Mainboard

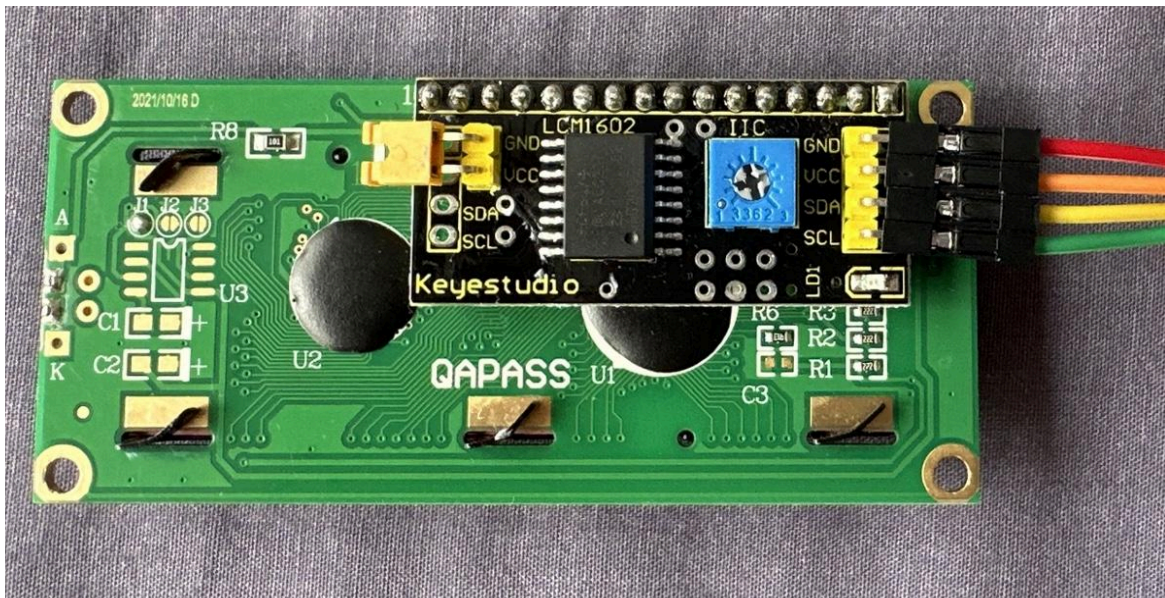


Display



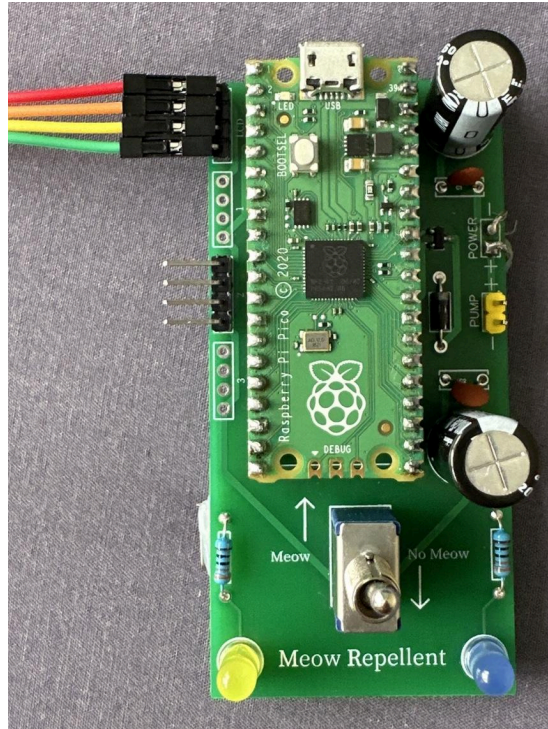

Mainboard

Pump to Mainboard

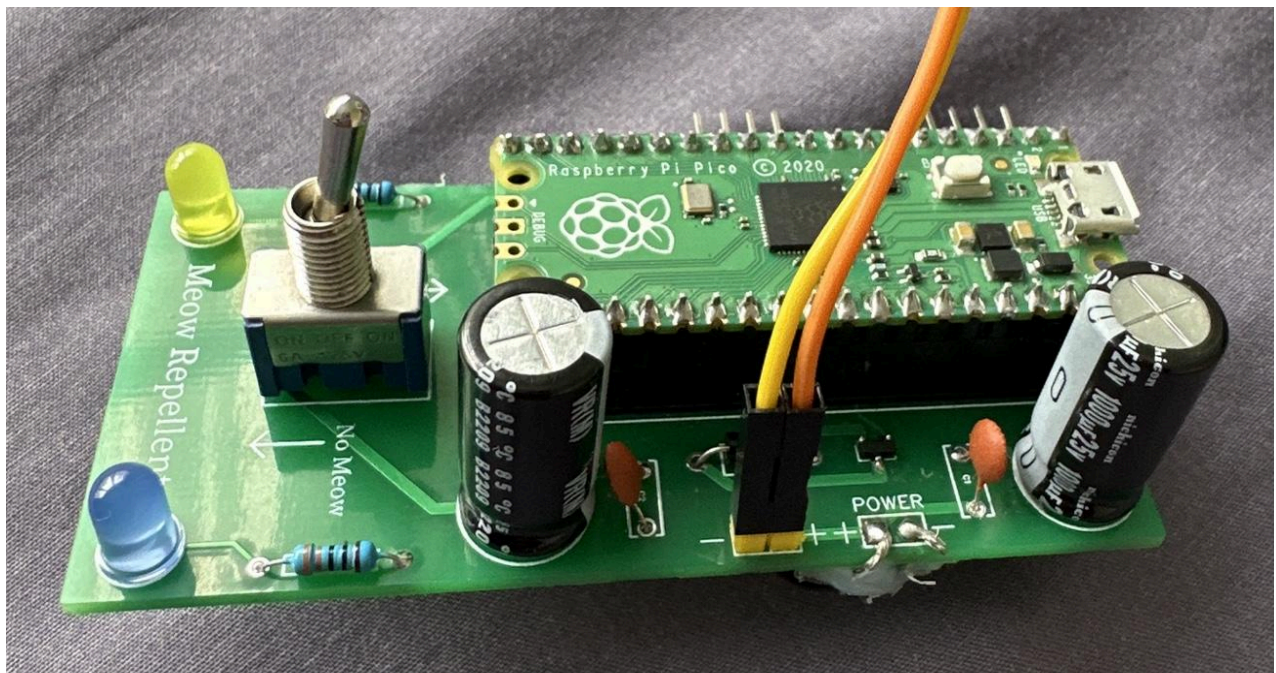

VERY IMPORTANT!

Make sure the orange wire is connected to + and yellow is connected to - .